

S.KEERTHANA 22BEC1503

EXP – 3: MULTISTAGE BJT

AIM: *To perform transient and AC analysis of a multi stage BJT using LTSpice software*

APPARATURS REQUIRED: *LTSpice software*

THEORY:

A Bipolar Junction Transistor (BJT) is a three-terminal device which consists of two pn-junctions formed by sandwiching either p-type or n-type semiconductor material between a pair of opposite type semiconductors. The primary function of BJT is to increase the strength of a weak signal, i.e., it acts as an amplifier. A BJT can also be used as a solid state switch in electronic circuits.

There are two types of BJTs –

- *NPN Transistor*

An npn-transistor is composed of two n-type semiconductor materials which are separated by a thin layer of p-type semiconductor. The two terminals viz. Emitter and Collector are taken out from the two n-type semiconductor and the Base terminal is from the p-type semiconductor.

- *PNP Transistor*


A pnp-transistor is composed of two p-type semiconductors which are separated by a thin layer of n-type material. The two terminals viz. Emitter and Collector are taken out from the two p-

type semiconductor layers and the Base terminal is from the n-type semiconductor. For the pnp-transistor, the conventional current flows into the emitter as indicated by the inward arrow.

PROCEDURE:


1. Build the circuit diagram of a double stage BJT in LTSpice.
2. Do transient analysis by setting stop time as 0.1 and time to start saving data as 0. Analyse the graph between input and output.
3. Do AC analysis by setting type of sweep as 'Decade', no. of points in decade as 10, start frequency as 10 and stop frequency as 10Meg. Observe the output graph.

TRANSIENT ANALYSIS:

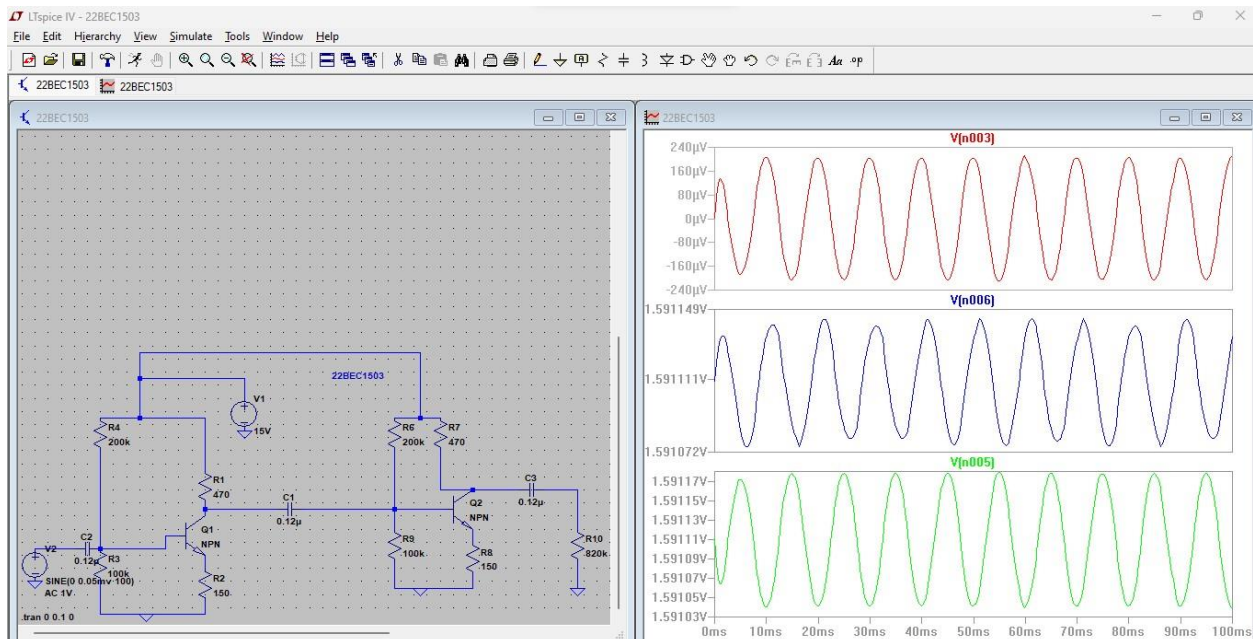


AC ANALYSIS:

WITHOUT BYPASS CAPACITOR :

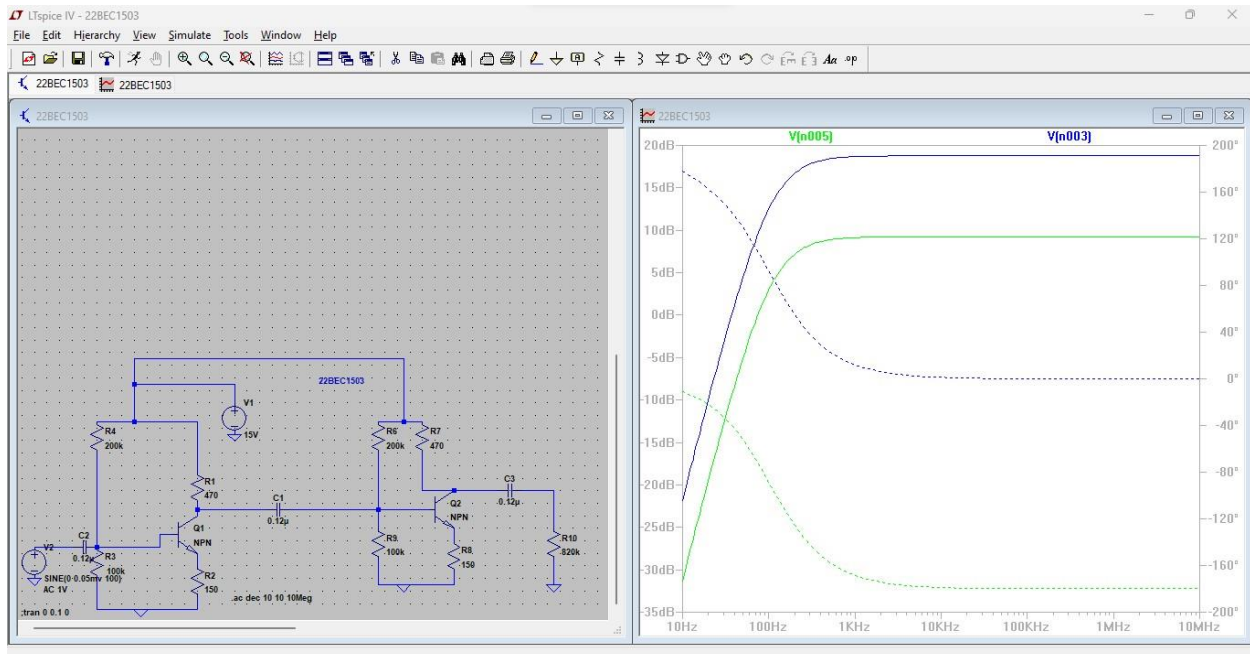

WITH BYPASS CAPACITOR:

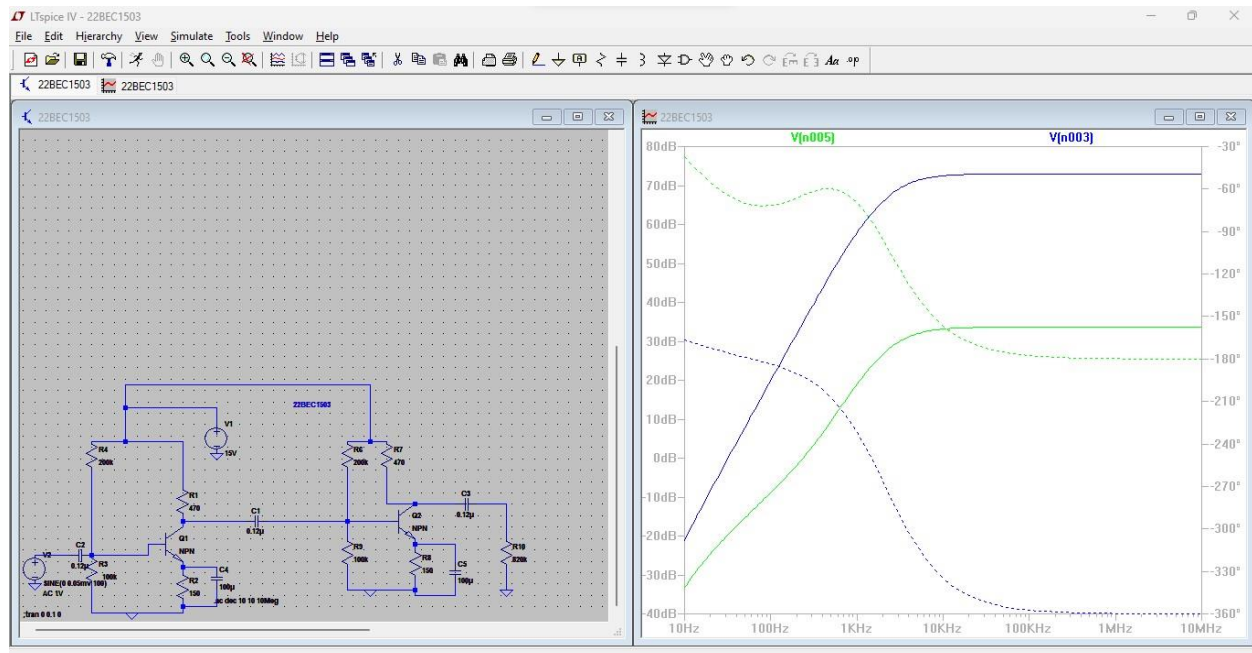

RESULT: Hence the transient and AC characteristics of a multi stage BJT are analyzed.